

Random Number Generator

Gholap Siddhesh Ashok
AI22BTECH11007

COMPONENTS USED

TABLE 0
COMPONENTS USED

Component	Value	Quantity
Breadboard		1
Seven segment display	Common Anode	1
Decoder	7447	1
Flip Flop	7474	2
X-OR Gate	7486	1
555 IC		1
Resistor	1K Ω	1
Capacitor	100nF	1
Capacitor	10nF	1
Jumper Wires		

Block Diagram

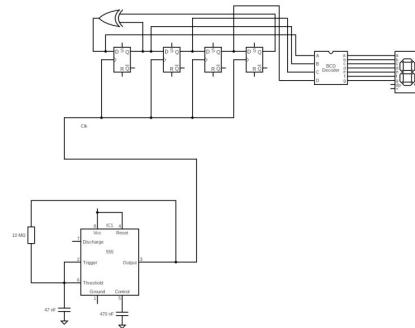


Figure 4: Block Diagram

Fig. 7. output

PROCEDURE

- 1) We connected the 555 timer circuit according to the figure
- 2) Then we connected Clock output of 555 timer circuit to the clock signal of D-Flip flops
- 3) Now we make the circuit for shift registers using a 4 D-Flip flops (using two 7474 IC's)
- 4) Then we connected XOR gate (7486 IC) according to the figure
- 5) then we connected the decoder (7447 IC) and connected its A,B,C,D with Q_0, Q_1, Q_2, Q_3 respectively as per the figure
- 6) Then we connected The seven segmented display and then connected it with the dceoder (7447 IC) according to the table and the figure
- 7) We connected all the independent parts with each other and then connected the power source

OUTPUT

Random numbers were displayed on the digital screen in a certain frequency.

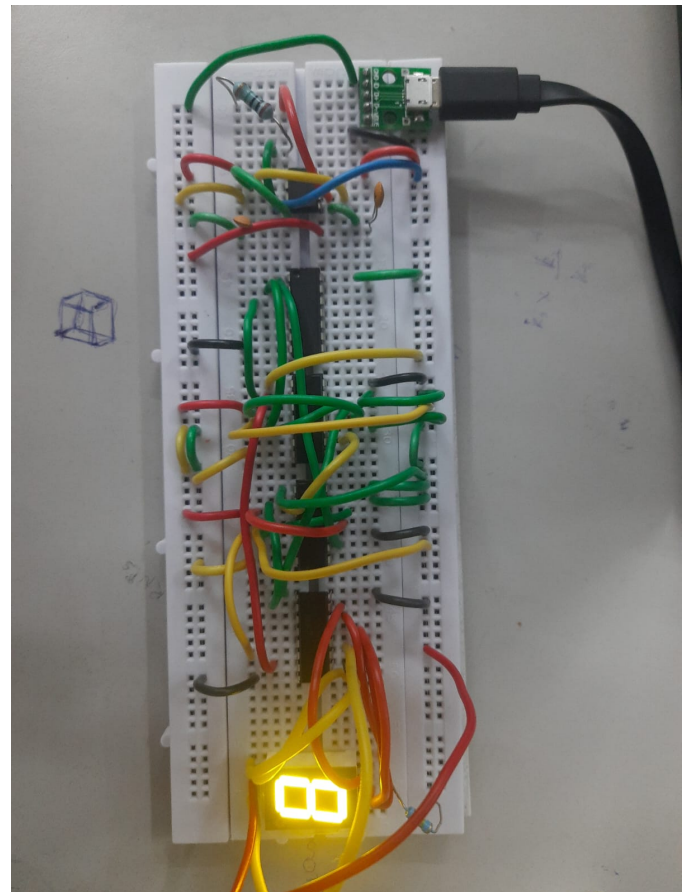


Fig. 7. output

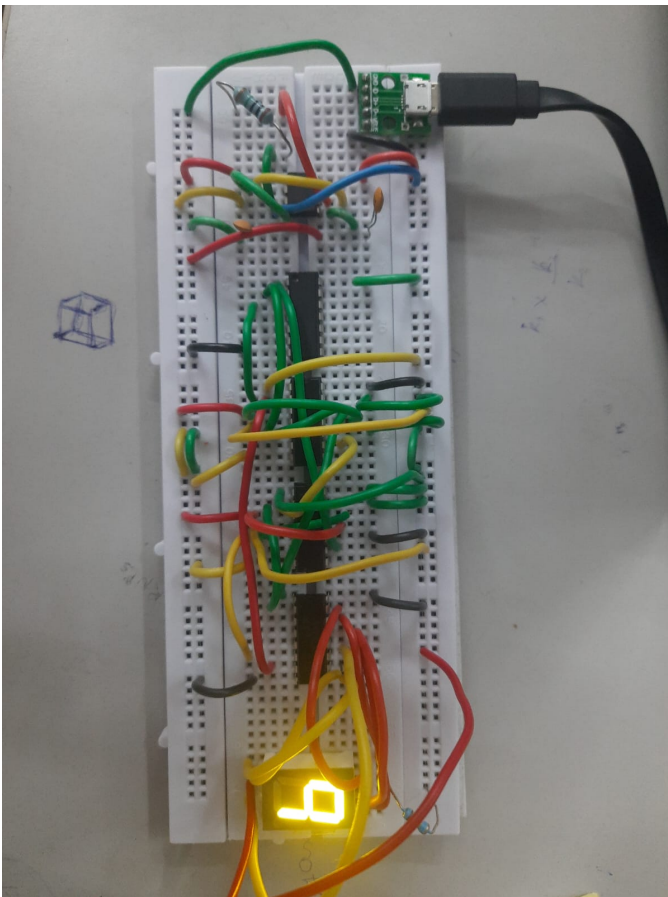


Fig. 7. output